

# Electricity (Y3&4)

## knowledge

Many household devices and appliances run on electricity. Some plug in to the mains and others run on batteries. (Name some.)

An electrical circuit consists of a cell or battery connected to a component using wires.

If there is a break in the circuit, a loose connection or a short circuit the component will not work.

A switch can be added to the circuit to turn the component on and off.

Metals are good conductors so they can be used as wires in a circuit.

Non-metallic solids are insulators except for graphite (pencil lead).

Water, if not completely pure, also conducts electricity.

Conductors allow electricity to pass through them, whereas insulators do not.

Make a series circuit that works and name the components in it.

Know whether a lamp will or will not light based on the circuit being complete or not.

**Children in year 4 do NOT need to use standard symbols for the components.**



## Subject Vocabulary

<b>cell/ battery</b>	a source of energy giving a push of energy to move the current
<b>wire</b>	something that connects different parts of a circuit
<b>bulb</b>	produces light if electricity is flowing
<b>switch</b>	starts and stops electricity flowing
<b>buzzer</b>	makes a noise if electricity is flowing
<b>circuit</b>	a roughly circular route that starts & finishes at the same cell
<b>series</b>	a closed circuit in which the current follows one path
<b>conductor</b>	allows electricity to pass through it
<b>insulator</b>	doesn't allow electricity to pass through it
<b>component</b>	a part of a circuit
<b>positive</b>	one side of a cell
<b>negative</b>	the opposite side of a cell
<b>short circuit</b>	where wires that are not supposed to come in contact with each other touch
<b>motor</b>	changes electrical energy to movement
<b>crocodile clip</b>	makes temporary electrical connection
<b>loose connection</b>	a cause of an imperfect circuit
<b>current</b>	the flow of an electric charge